

# CS2100 Tutorial 6

Boolean Algebra, Logic Gates & Simplification

take k-map sheet in front  
will start at :05 as usual

# Recap

- K-maps
- minterm and Maxterm
- Boolean Algebra laws

(Announcement: A1, A2, midterms)

# Overview

Q1) Consensus theorem

Q2) Simplification

Q3) Intro to K-maps

Q4) More K-maps




# Q1. Consensus theorem

$$x \cdot y + x' \cdot z + y \cdot z = x \cdot y + x' \cdot z$$

Note:  
The dot is important!

# Q1. Consensus theorem

$$x \cdot y + x' \cdot z + y \cdot z = x \cdot y + x' \cdot z$$

		$y$			
					
		0	1	1	0
$x$		0	0	1	1
				$z$	

# Q1. Consensus theorem

$$x \cdot y + x' \cdot z + y \cdot z = x \cdot y + x' \cdot z$$

		$y$		
		}		
	0	1	1	0
$x$	0	0	1	1
		$z$		
		}		

# Q1. Consensus theorem

$$x \cdot y + x' \cdot z + y \cdot z = x \cdot y + x' \cdot z$$

		$y$		
$x$	0	1	1	0
	0	0	1	1
		$z$		

$$\begin{aligned} x \cdot y + x' \cdot z + y \cdot z &= x \cdot y + x' \cdot z + 1 \cdot y \cdot z \\ &= x \cdot y + x' \cdot z + (x + x') \cdot y \cdot z \\ &= x \cdot y + x' \cdot z + x \cdot y \cdot z + x' \cdot y \cdot z \\ &= x \cdot y + x \cdot y \cdot z + x' \cdot z + x' \cdot y \cdot z \\ &= (x \cdot y + x \cdot y \cdot z) + (x' \cdot z + x' \cdot y \cdot z) \\ &= x \cdot y + x' \cdot z \end{aligned}$$

[identity law]

[complement law]

[distributive law]

[commutative law]

[associative law]

[absorption theorem 1]

## Q2a. Simplifying to SOP

$$F(x,y,z) = (x+y \cdot z') \cdot (y'+y) + x' \cdot (y \cdot z' + y)$$

$$= (x+y \cdot z') \cdot 1 + x' \cdot (y \cdot z' + y) \quad \text{(by the complement law)}$$

$$= (x+y \cdot z') + x' \cdot (y \cdot z' + y) \quad \text{(by the identity law)}$$

$$= x + y \cdot z' + x' \cdot y \quad \text{(by absorption theorem 1)}$$

$$= x + x' \cdot y + y \cdot z' \quad \text{(by the commutative law)}$$

$$= x + y + y \cdot z' \quad \text{(by absorption theorem 2)}$$

$$= x + y \quad \text{(by absorption theorem 1)}$$



## Q2b. Simplifying to SOP

$$G(p,q,r,s) = \prod M(5, 9, 13)$$

$$5 = (0101)_2; 9 = (1001)_2; 13 = (1101)_2$$

## Q2b. Simplifying to SOP

$$G(p,q,r,s) = \prod M(5, 9, 13)$$

$$5 = (0101)_2; 9 = (1001)_2; 13 = (1101)_2$$

$$= (p+q'+r+s') \cdot (p'+q+r+s') \cdot (p'+q'+r+s') \text{ (by definition of maxterms)}$$

## Q2b. Simplifying to SOP

$$G(p,q,r,s) = \prod M(5, 9, 13)$$

$$5 = (0101)_2; 9 = (1001)_2; 13 = (1101)_2$$

$$= (p+q'+r+s') \cdot (p'+q+r+s') \cdot (p'+q'+r+s') \quad (\text{by definition of maxterms})$$

$$= ((p \cdot p') + (q'+r+s')) \cdot (p'+q+r+s') \quad (\text{by the distributive law})$$

$$\begin{aligned} & (p+(q'+r+s')) \cdot (p'+(q'+r+s')) \\ &= (p \cdot p') + (q'+r+s') \end{aligned}$$

Distributive law:

$$\begin{aligned} A + (B \cdot C) &= (A+B) \cdot (A+C) \\ \text{or } (B \cdot C) + A &= (B+A) \cdot (C+A) \end{aligned}$$

## Q2b. Simplifying to SOP

Absorption theorem 2:

$$A \cdot (A' + B) = A \cdot B$$

$$G(p, q, r, s) = \prod M(5, 9, 13)$$

$$q' \cdot (p' + q) = q' \cdot (q + p') = q' \cdot p' = p' \cdot q'$$

$$= (p + q' + r + s') \cdot (p' + q + r + s') \cdot (p' + q' + r + s') \quad (\text{by definition of maxterms})$$

$$= ((p \cdot p') + (q' + r + s')) \cdot (p' + q + r + s') \quad (\text{by the distributive law})$$


$$= (0 + (q' + r + s')) \cdot (p' + q + r + s') \quad (\text{by the complement law})$$

$$= (q' + r + s') \cdot (p' + q + r + s') \quad (\text{by the identity law})$$

$$= (q' \cdot (p' + q)) + (r + s') \quad (\text{by the distributive law})$$

$$= p' \cdot q' + r + s' \quad (\text{by absorption 2})$$

## Q3. K-maps

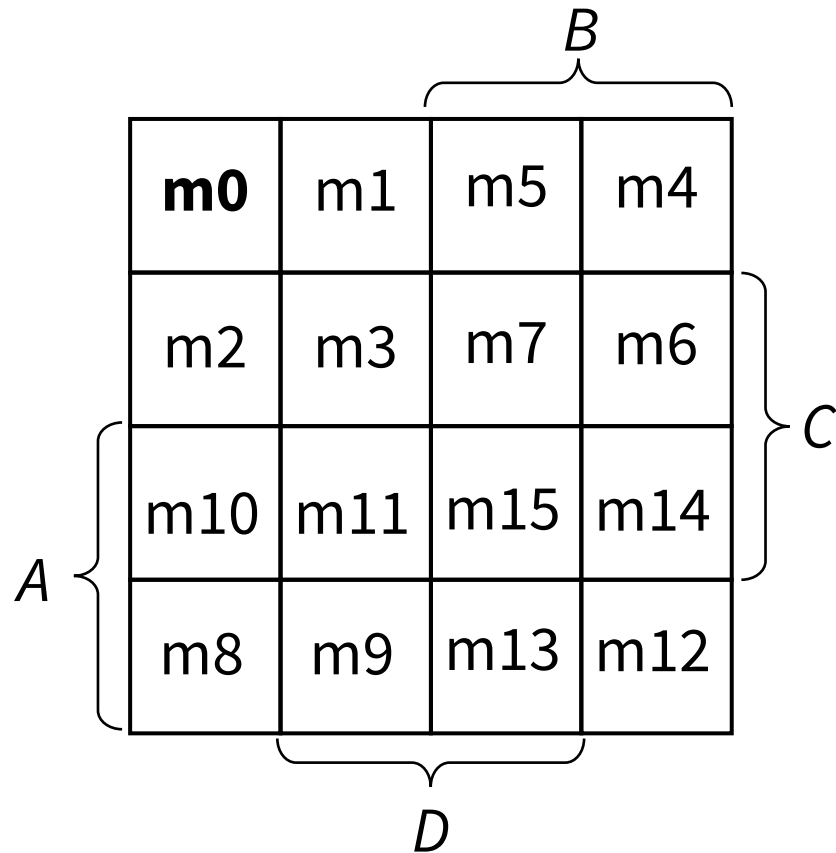

m1: 0001 =  $A' \cdot B' \cdot C' \cdot D$



m2: 0010 =  $A' \cdot B' \cdot C \cdot D'$

m3: 0011 =  $A' \cdot B' \cdot C \cdot D$

## Q3. K-maps

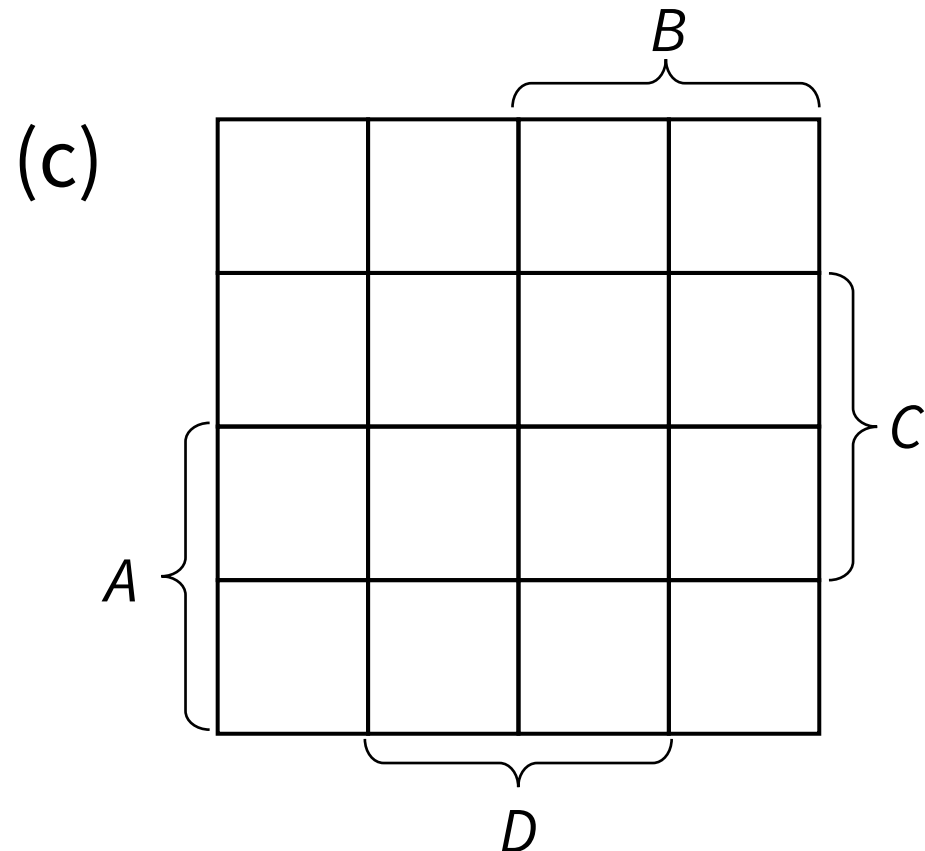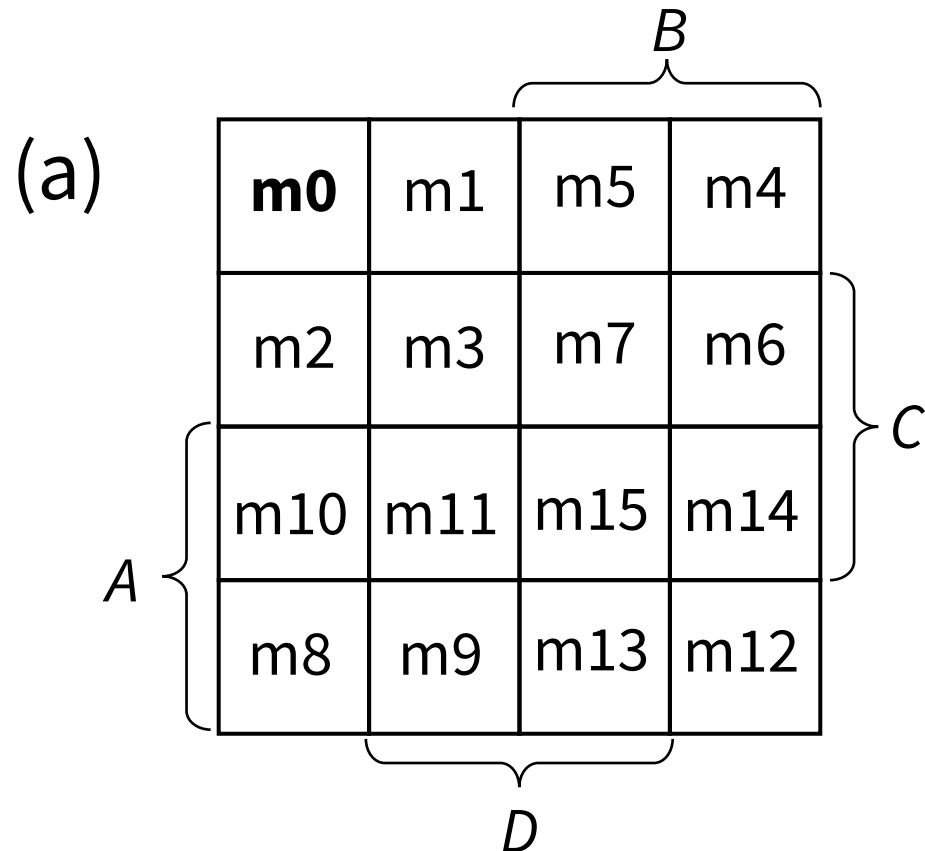(b)  $T(A,B,C,D) = \prod M(3,7,8,10,12,13) \cdot X(6,11,14,15).$

$T(A,B,C,D) = \Sigma m(0,1,2,4,5,9) + X(6,11,14,15).$



## Q3. K-maps

(b)  $T(A,B,C,D) = \prod M(3,7,8,10,12,13) \cdot X(6,11,14,15).$

$T(A,B,C,D) = \Sigma m(0,1,2,4,5,9) + X(6,11,14,15).$

(a)

$B$			
<b>m0</b>	m1	m5	m4
m2	m3	m7	m6
m10	m11	m15	m14
m8	m9	m13	m12

$A$  {  $C$   $D$

(c)

$B$			
1	1	1	1
1	0	0	X
0	X	X	X
0	1	0	0

$A$  {  $C$   $D$

# Q3. K-maps

(b)  $T(A,B,C,D) = \prod M(3,7,8,10,12,13) \cdot X(6,11,14,15).$

$T(A,B,C,D) = \Sigma m(0,1,2,4,5,9) + X(6,11,14,15).$

(a)

				$B$	
$A$		<b>m0</b>	m1	m5	m4
		m2	m3	m7	m6
		m10	m11	m15	m14
		m8	m9	m13	m12
		$D$			
		$C$			

(c)


				$B$	
$A$		1	1	1	1
		1	0	0	X
		0	X	X	X
		0	1	0	0
		$D$			
		$C$			



# Q3. K-maps


(d) How many PIs?

(e) How many EPIs?

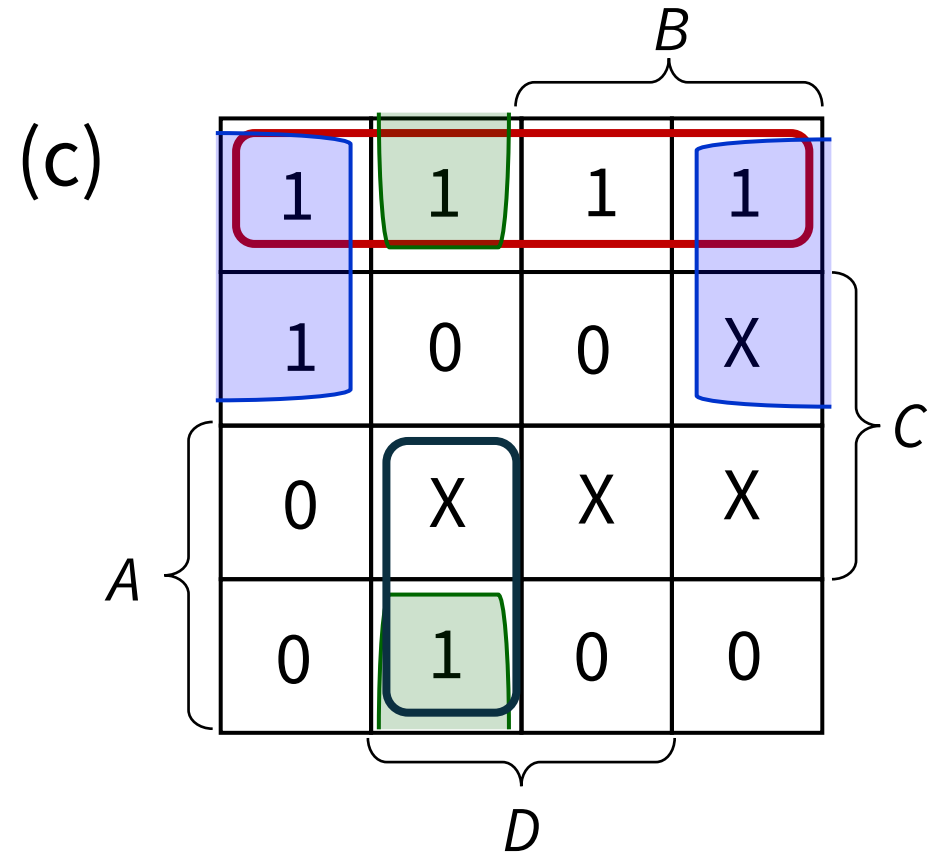

## Q3. K-maps

(f) Simplified SOP expression:

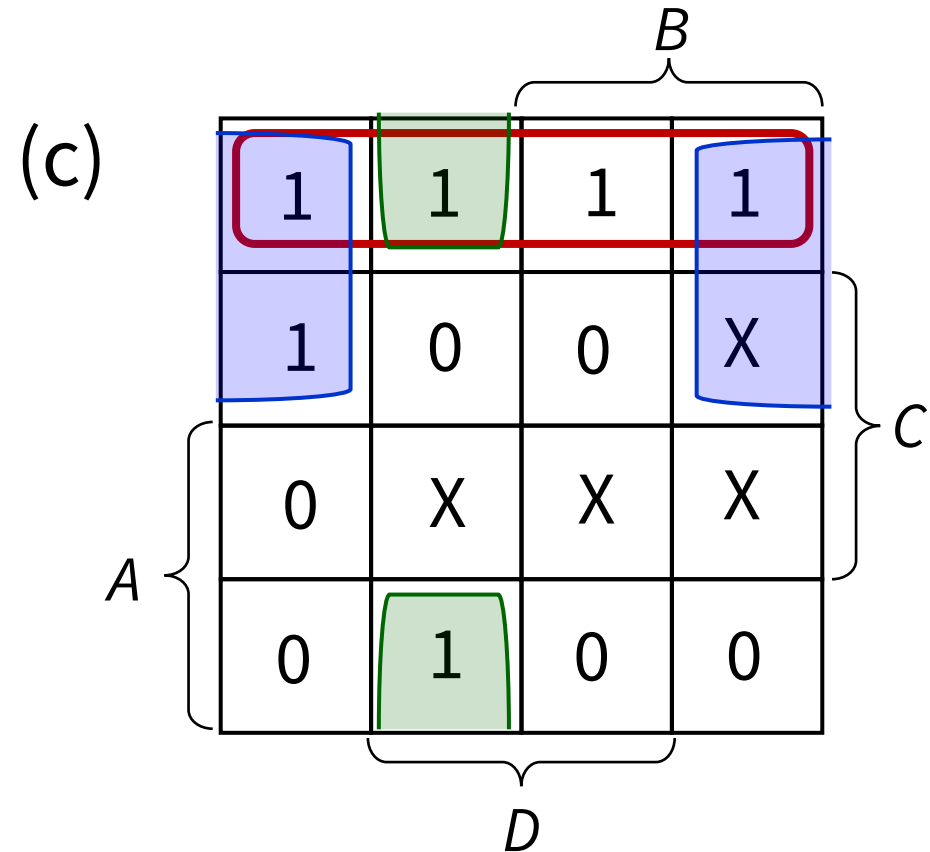


## Q3. K-maps

(f) Simplified SOP expression:

$$A' \cdot D' + A' \cdot C' + B' \cdot C' \cdot D$$


or
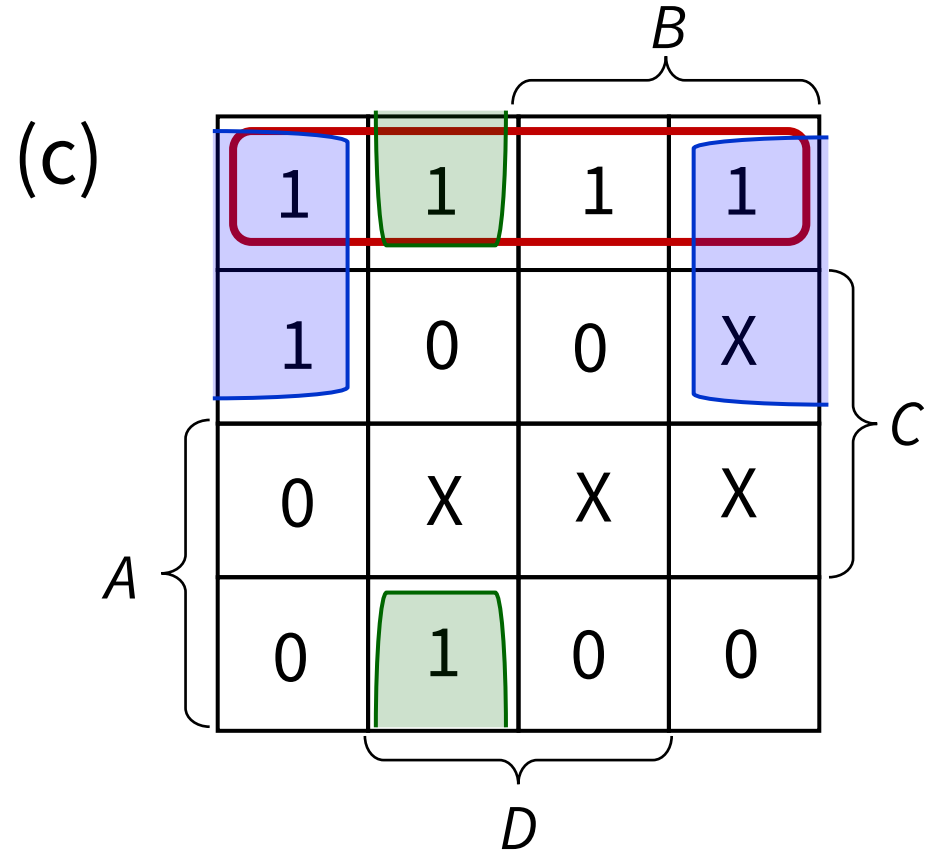
$$A' \cdot D' + A' \cdot C' + A \cdot B' \cdot D$$




# Q3. K-maps

(g) K-map for  $T'$ :

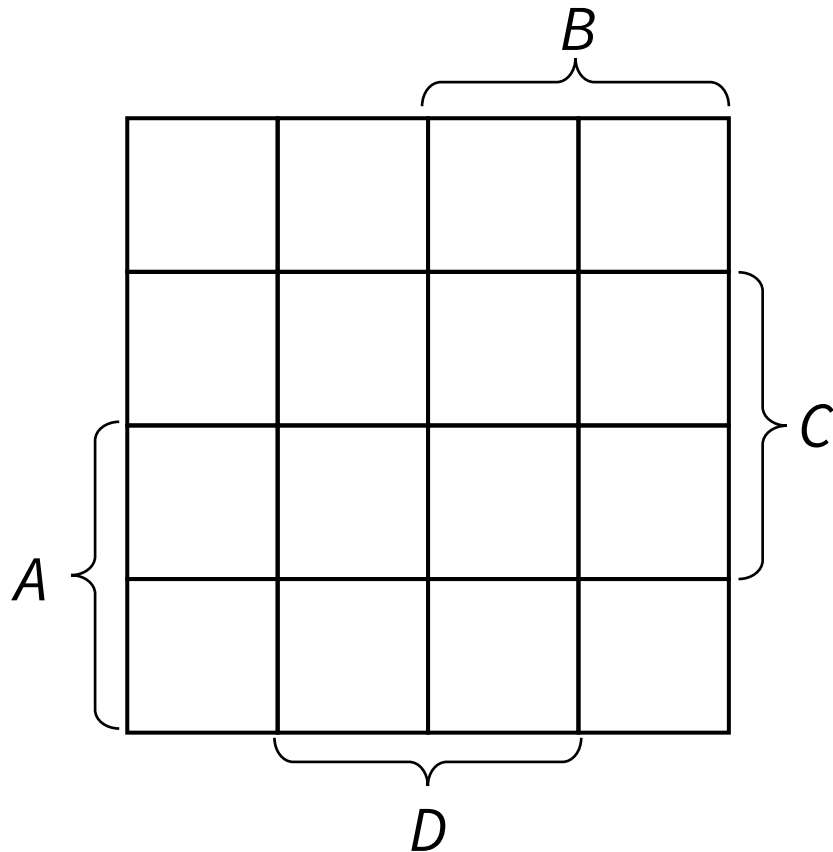

(c) K-map for  $T$ :

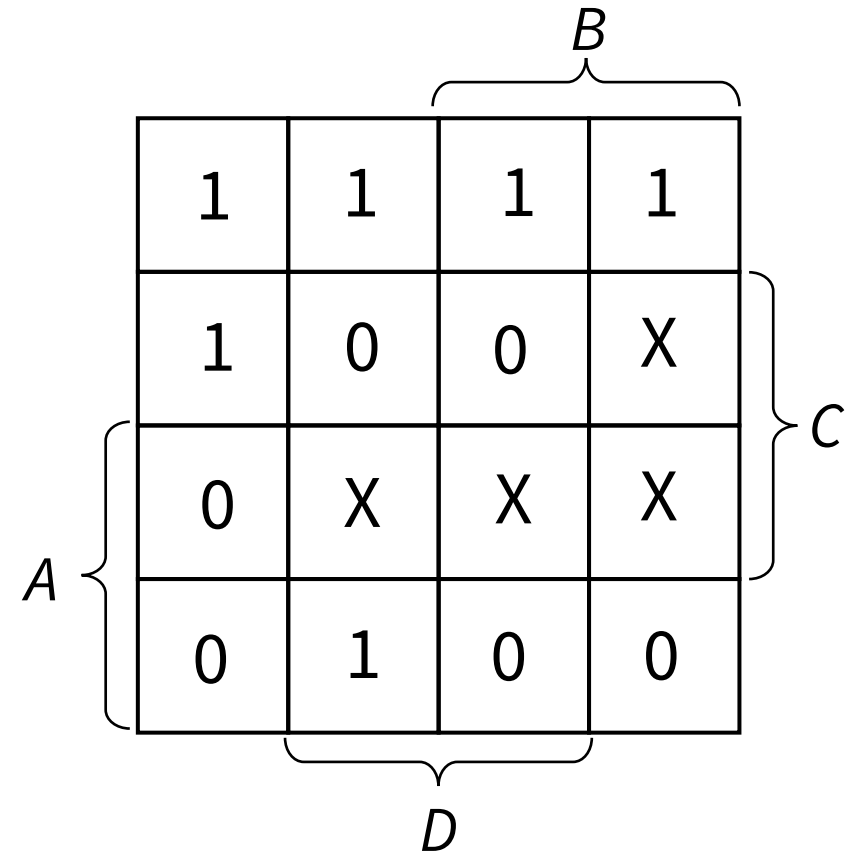

# Q3. K-maps

(g) K-map for  $T'$ :

				$B$							
				{							
{											
	0				0						
	0				1						
	1				X						
1				X				{	$C$		
0				1							
1				1							
1				1							
				{							
				$D$							

(c) K-map for  $T$ :

				$B$				
				{				
{					1	1	1	1
					1	0	0	X
					0	X	X	X
					0	1	0	0
				{				$C$
				$D$				

# Q3. K-maps

(g) K-map for  $T'$ :


$B$					
0	0	0	0		
0	1	1	X	$C$	
1	X	X	X		
1	0	1	1	$D$	
$A$					

(c) K-map for  $T$ :

$B$					
1	1	1	1		
1	0	0	X	$C$	
0	X	X	X		
0	1	0	0	$D$	
$A$					

## Q3. K-maps

(g) K-map for  $T'$ :

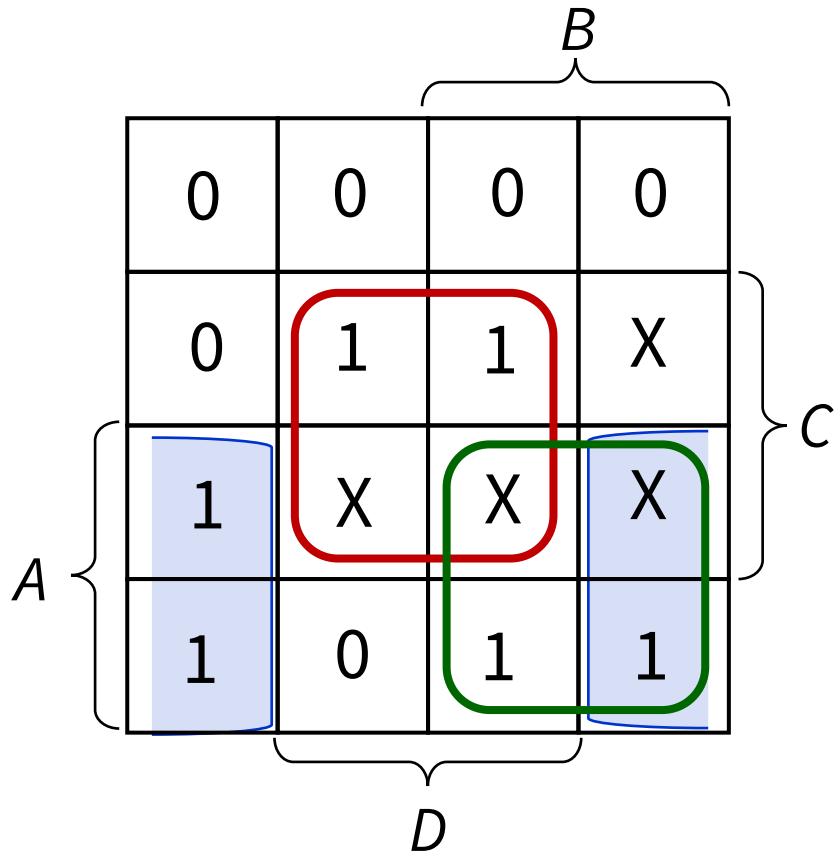


(g) Simplified POS expression:

$T' =$

$T =$

# Q3. K-maps

(g) K-map for T':

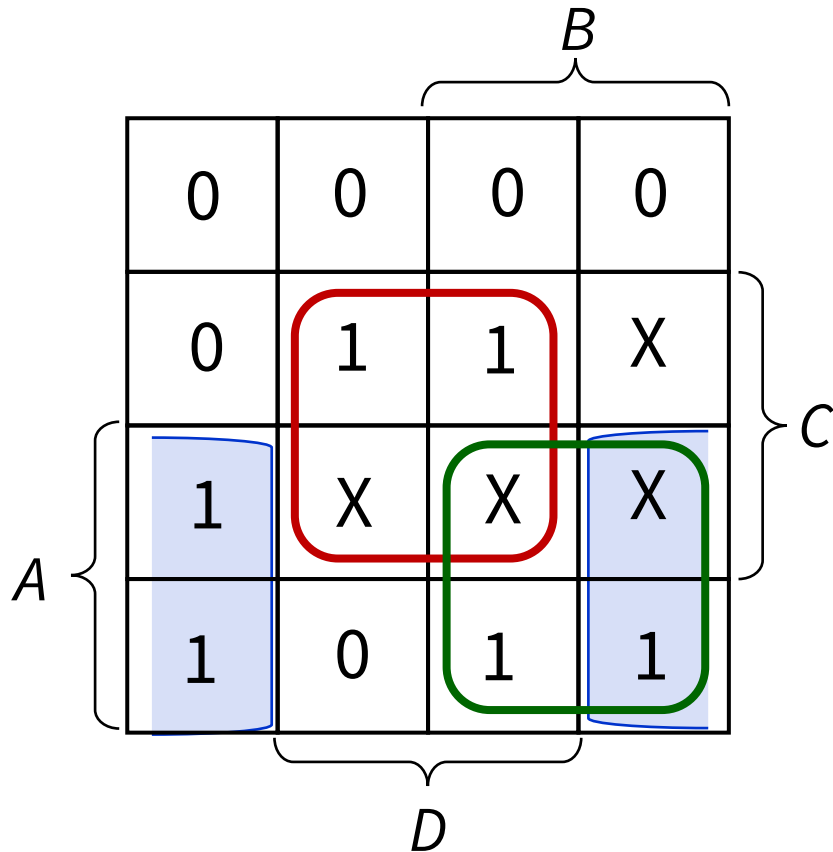

(g) Simplified POS expression:

$$T' = A \cdot D' + C \cdot D + A \cdot B$$

$$T = (A \cdot D' + C \cdot D + A \cdot B)'$$

$$= (A' + D) \cdot (C' + D') \cdot (A' + B')$$



# Q3. K-maps



2-level AND-OR circuit:

Note: draw nicely :)

- Rulers for lines
- Thick dots for wire junctions
- Unfilled circle on NAND gates

2-level NAND circuit:
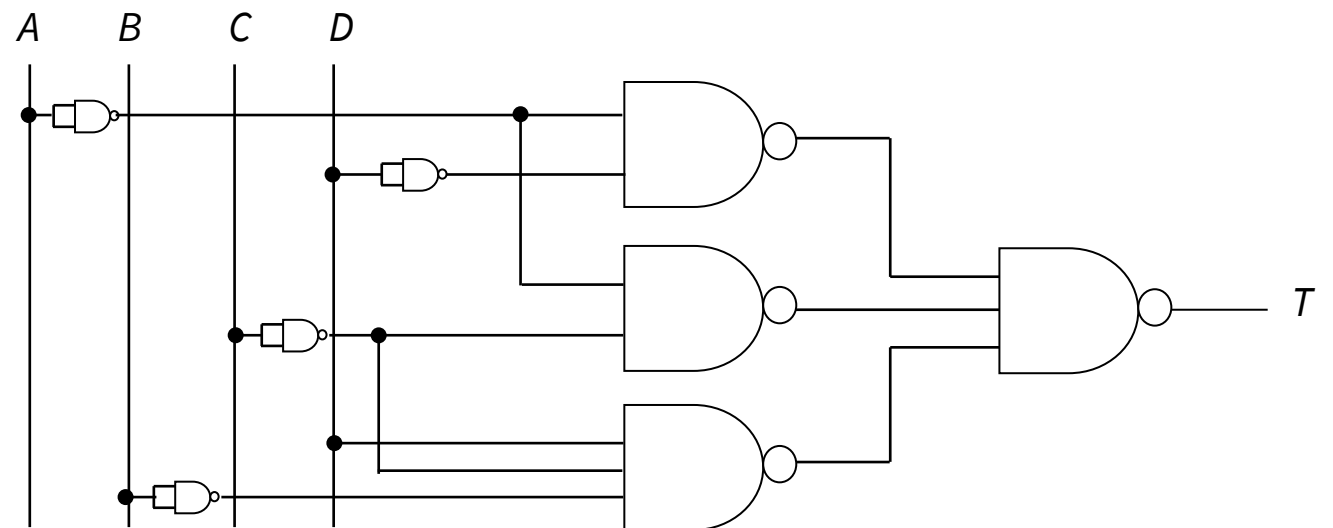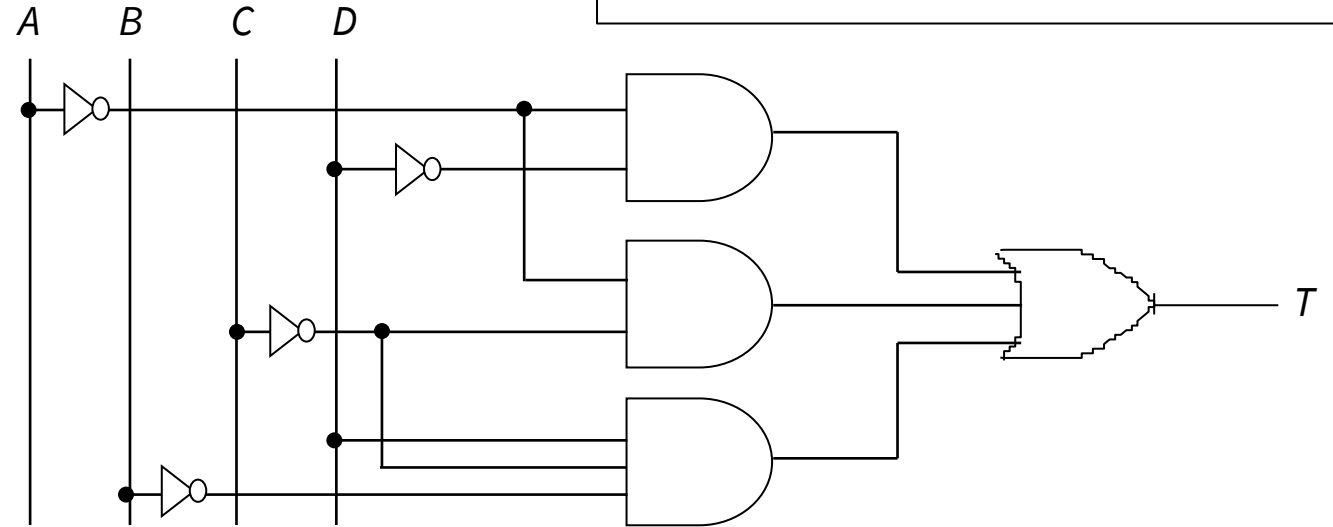
$$T = A' \cdot D' + A' \cdot C' + B' \cdot C' \cdot D$$



# Q4. Circuits with don't-cares

$KL, MN$  are 2-bit unsigned integers.

$X(K,L,M,N)$

= 1 if  $KL = MN$   
or 0 otherwise

$Y(K,L,M,N)$

= 1 if  $KL \leq MN$   
or 0 otherwise

$Z(K,L,M,N)$

= 1 if  $KLM < LMN$   
or 0 otherwise

Assume input 0000  
will not occur.

$K$	$L$	$M$	$N$	$X$	$Y$	$Z$
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			

$K$	$L$	$M$	$N$	$X$	$Y$	$Z$
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

# Q4. Circuits with don't-cares

$X(K,L,M,N)$

= 1 if  $KL = MN$   
or 0 otherwise

$Y(K,L,M,N)$

= 1 if  $KL \leq MN$   
or 0 otherwise

$Z(K,L,M,N)$

= 1 if  $KLM < LMN$   
or 0 otherwise

Assume input 0000  
will not occur.


$K$	$L$	$M$	$N$	$X$	$Y$	$Z$
0	0	0	0	d	d	d
0	0	0	1	0	1	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	1	1	1
0	1	1	0	0	1	1
0	1	1	1	0	1	1

$K$	$L$	$M$	$N$	$X$	$Y$	$Z$
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	1	0
1	0	1	1	0	1	0
1	1	0	0	0	0	0
1	1	0	1	0	0	0
1	1	1	0	0	0	0
1	1	1	1	1	1	0

# Q4. Circuits with don't-cares

$K$	$L$	$M$	$N$	$X$	$Y$	$Z$
0	0	0	0	d	d	d
0	0	0	1	0	1	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	1	1	1
0	1	1	0	0	1	1
0	1	1	1	0	1	1

$K$	$L$	$M$	$N$	$X$	$Y$	$Z$
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	1	0
1	0	1	1	0	1	0
1	1	0	0	0	0	0
1	1	0	1	0	0	0
1	1	1	0	0	0	0
1	1	1	1	1	1	0

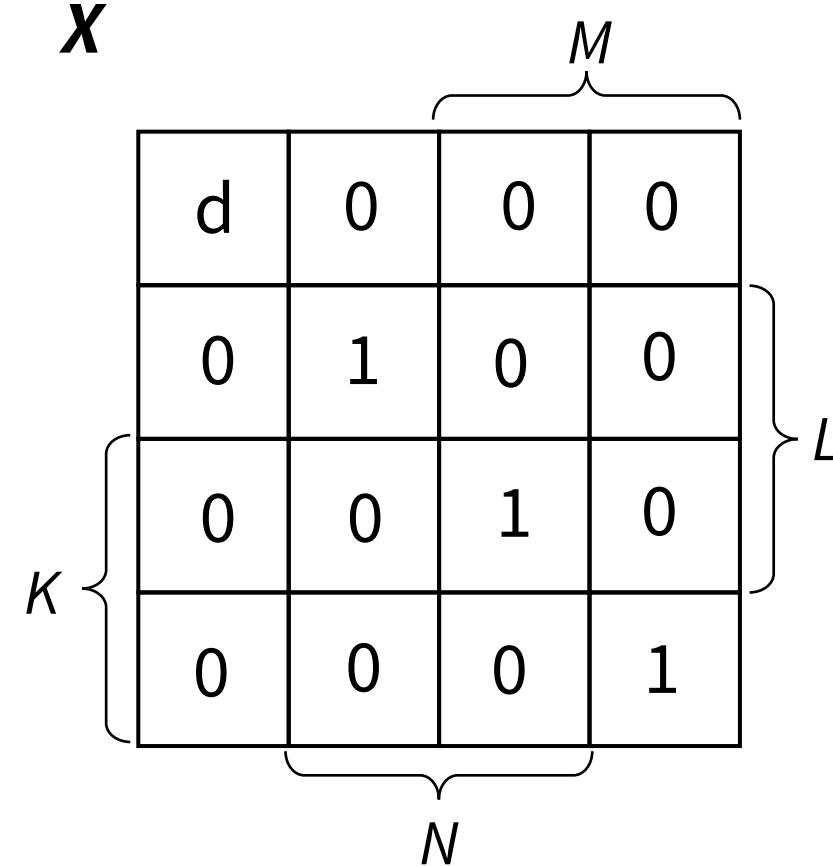


$$X = K' \cdot L \cdot M' \cdot N + K \cdot L' \cdot M \cdot N' + K \cdot L \cdot M \cdot N$$

$$KLMN = 0000 \rightarrow X = 0$$

# Q4. Circuits with don't-cares

$K$	$L$	$M$	$N$	$X$	$Y$	$Z$
0	0	0	0	d	d	d
0	0	0	1	0	1	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	1	1	1
0	1	1	0	0	1	1
0	1	1	1	0	1	1

$K$	$L$	$M$	$N$	$X$	$Y$	$Z$
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	1	0
1	0	1	1	0	1	0
1	1	0	0	0	0	0
1	1	0	1	0	0	0
1	1	1	0	0	0	0
1	1	1	1	1	1	0

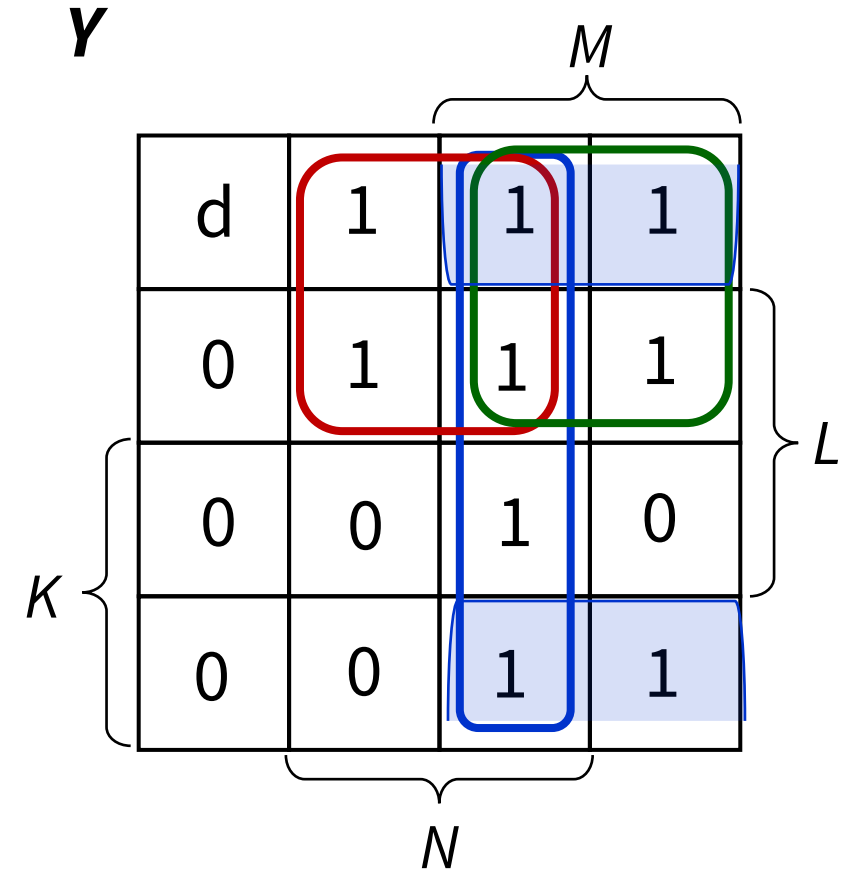


$$Y = M \cdot N + K' \cdot N + K' \cdot M + L' \cdot M$$

$$KLMN = 0000 \rightarrow Y = 0$$

# Q4. Circuits with don't-cares

<i>K</i>	<i>L</i>	<i>M</i>	<i>N</i>	<i>X</i>	<i>Y</i>	<i>Z</i>
0	0	0	0	d	d	d
0	0	0	1	0	1	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	1	1	1
0	1	1	0	0	1	1
0	1	1	1	0	1	1

<i>K</i>	<i>L</i>	<i>M</i>	<i>N</i>	<i>X</i>	<i>Y</i>	<i>Z</i>
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	1	0
1	0	1	1	0	1	0
1	1	0	0	0	0	0
1	1	0	1	0	0	0
1	1	1	0	0	0	0
1	1	1	1	1	1	0

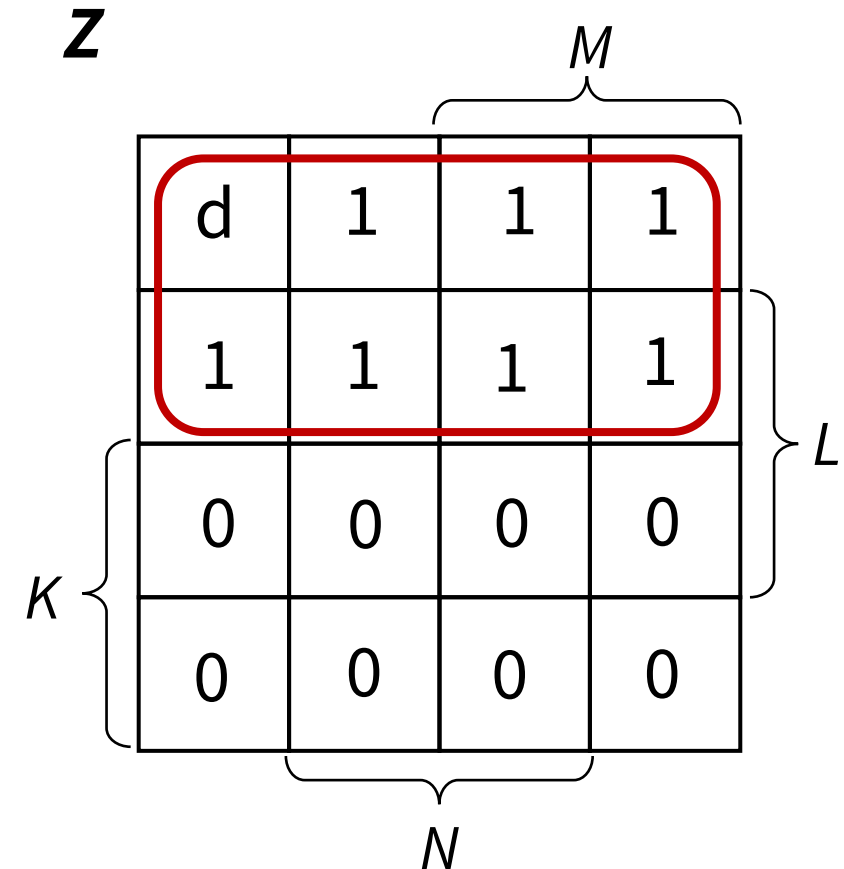

$$Z = K'$$

$$KLMN = 0000 \rightarrow Z = 1$$

# End of Tutorial 6

- Slides uploaded on [github.com/theodoreleebrant/TA-2425S1](https://github.com/theodoreleebrant/TA-2425S1)
- Email: [theo@comp.nus.edu.sg](mailto:theo@comp.nus.edu.sg)
- Anonymous feedback:  
[bit.ly/feedback-theodore](https://bit.ly/feedback-theodore)  
(or scan on the right)



(Also reminder for me to take attendance)